



Single Board Computer Design


8086 DESIGNING

WWW.BHARATACHARYAEDUCATION.COM



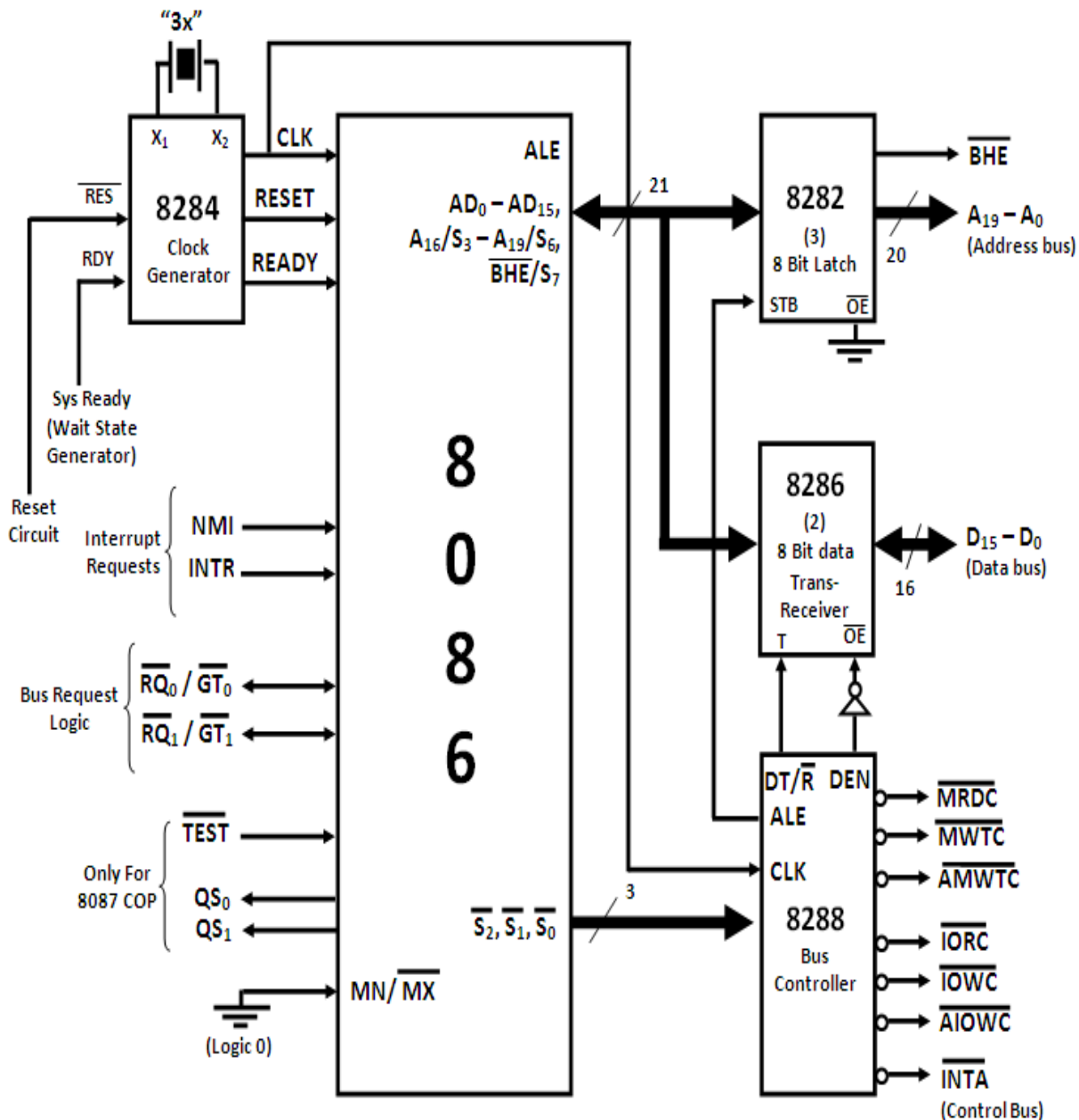- Q1) Design an 8086 based Maximum Mode system working at 6 MHz having the following:**
32KB EPROM using 16KB chips,
128KB RAM using 32KB chips,
Two 16-bit input and two 16-bit output ports all interrupt driven (20m)

Soln: Show 8086 max mode config with a crystal of 18 MHZ.





Memory Calculations:

EPROM:

Required = 32 KB, Available = 16 KB

No. of chips = 2 chips.

Starting address of EPROM is calculated as:

FFFFFH – (Space required by total EPROM of 32 KB)

$$\begin{array}{r} \text{F F F F F H} \\ - \text{7 F F F H} \\ \hline \text{F 8 0 0 0 H} \end{array}$$

Size of a single EPROM chip = 16 KB

$$\begin{aligned} &= 16 \times 1\text{KB} = 2^4 \times 2^{10} \\ &= 2^{14} \\ &= \underline{14} \text{ address lines} \end{aligned}$$

$$= \underline{\text{(A14 ... A1)}}$$

RAM:

Required = 128 KB, Available = 32 KB

No. of chips = 4 chips.

Starting address of RAM is: 00000H

Size of a single RAM chip = 32 KB

$$\begin{aligned} &= 32 \times 1\text{KB} = 2^5 \times 2^{10} \\ &= 2^{15} \\ &= \underline{15} \text{ address lines} \end{aligned}$$


$$= \underline{\text{(A15 ... A1)}}$$

📞 **For doubts contact Bharat Sir at 98204 08217**



MEMORY MAP

Memory Chip	Address Bus																				Memory Address
	A19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
RAM 1 (LB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	00000H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	0FFFEH
RAM 2 (HB)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	00001H
	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0FFFFH
RAM 3 (LB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	10000H
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1FFFEH
RAM 4 (HB)	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	10001H
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1FFFFH
EPORM 1 (LB)	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	F8000H
	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	FFFFEH
EPORM 2 (HB)	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	F8001H
	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	FFFFFH

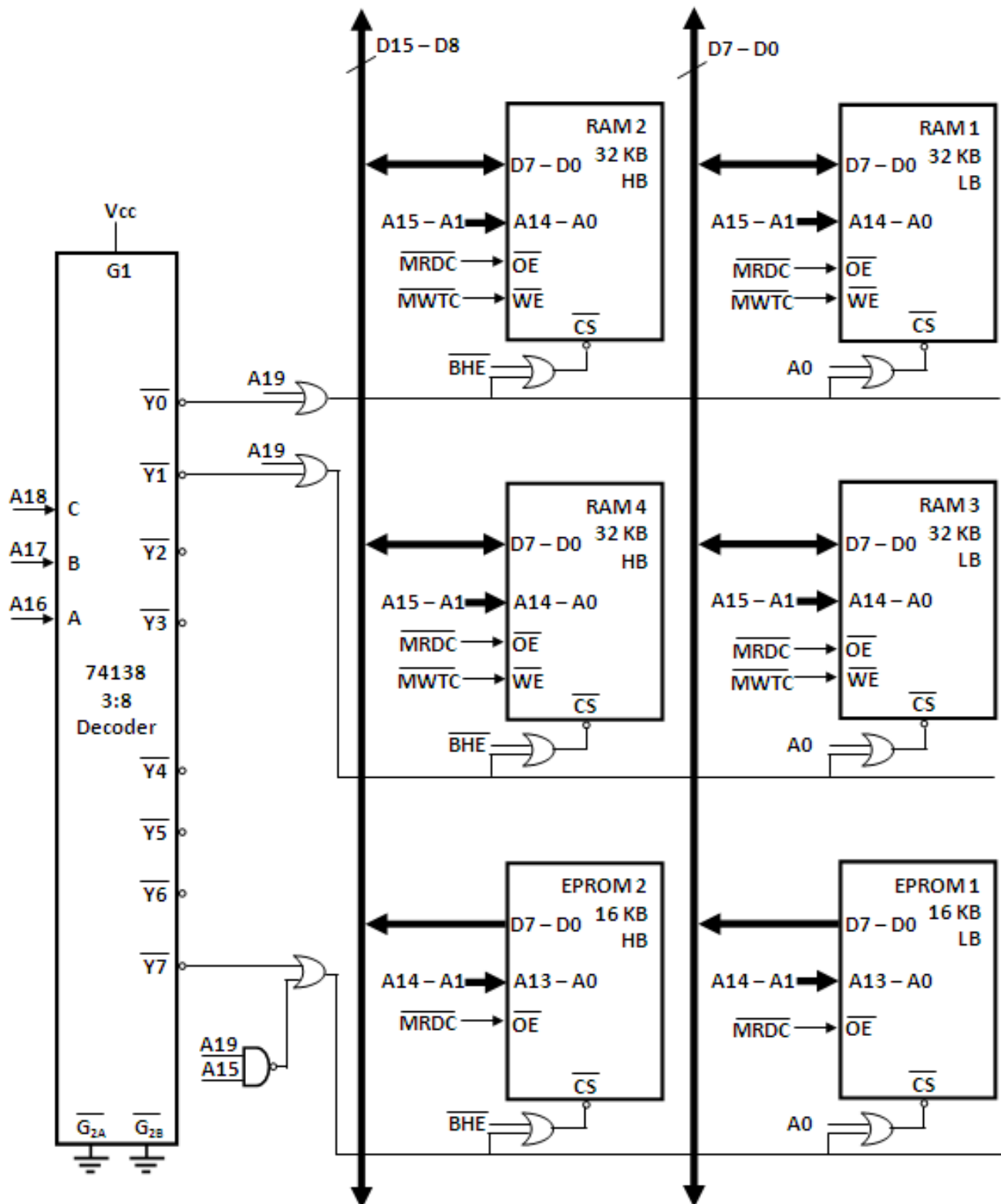



I/O Map

I/O Port	Address Bus																I/O Address
	A15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	A0	
8255 LB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	0060H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	0	0062H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	0	0064H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	0	0066H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	1	0061H
Port B	0	0	0	0	0	0	0	0	0	1	1	0	0	0	1	1	0063H
Port C	0	0	0	0	0	0	0	0	0	1	1	0	0	1	0	1	0065H
C Word	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1	1	0067H
8255 LB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0080H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	0082H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	0	0084H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	0	0086H
8255 HB																	
Port A	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0081H
Port B	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	1	0083H
Port C	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1	0085H
C Word	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1	1	0087H

